

4 - bit adders

4 Bit Ripple Carry Adder in Verilog

Structural Model : Half Adder

```
module half_adder(  
    output S,C,  
    input A,B  
);  
    xor(S,A,B);  
    and(C,A,B);  
endmodule
```

Structural Model : Full Adder

```
module full_adder(  
    output S,Cout,  
    input A,B,Cin  
);  
    wire s1,c1,c2;  
    half_adder HA1(s1,c1,A,B);  
    half_adder HA2(S,c2,s1,Cin);  
    or OG1(Cout,c1,c2);  
endmodule
```

Structural Model : 4 Bit Ripple Carry Adder

```
module ripple_adder_4bit(  
    output [3:0] Sum,  
    output Cout,  
    input [3:0] A,B,  
    input Cin  
);  
    wire c1,c2,c3;  
    full_adder FA1(Sum[0],c1,A[0],B[0],Cin),  
    FA2(Sum[1],c2,A[1],B[1],c1),
```

```

        FA3(Sum[2],c3,A[2],B[2],c2),
        FA4(Sum[3],Cout,A[3],B[3],c3);

endmodule

```

Test Bench : 4 Bit Ripple Carry Adder

```

module test_ripple_adder_4bit;
    // Inputs
    reg [3:0] A;
    reg [3:0] B;
    reg Cin;
    // Outputs
    wire [3:0] Sum;
    wire Cout;
    // Instantiate the Unit Under Test (UUT)
    ripple_adder_4bit uut (
        .Sum(Sum),
        .Cout(Cout),
        .A(A),
        .B(B),
        .Cin(Cin)
    );
    initial begin
        // Initialize Inputs
        A = 0;
        B = 0;
        Cin = 0;
        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
        A=4'b0001;B=4'b0000;Cin=1'b0;
        #10 A=4'b1010;B=4'b0011;Cin=1'b0;
        #10 A=4'b1101;B=4'b1010;Cin=1'b1;
    end
    initial begin
        $monitor("time=", $time, , "A=%b B=%b Cin=%b : Sum=%b Cout=%b", A, B, Cin, Sum, Cout);
    end
end

```

```
Endmodule
```

4 Bit Carry Look Ahead Adder in Verilog

DataFlow Model : 4 Bit CLA

```
module CLA_4bit(  
    output [3:0] S,  
    output Cout,PG,GG,  
    input [3:0] A,B,  
    input Cin  
);  
    wire [3:0] G,P,C;  
  
    assign G = A & B; //Generate  
    assign P = A ^ B; //Propagate  
    assign C[0] = Cin;  
    assign C[1] = G[0] | (P[0] & C[0]);  
    assign C[2] = G[1] | (P[1] & G[0]) | (P[1] & P[0] & C[0]);  
    assign C[3] = G[2] | (P[2] & G[1]) | (P[2] & P[1] & G[0]) |  
        (P[2] & P[1] & P[0] & C[0]);  
    assign Cout = G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) |  
        (P[3] & P[2] & P[1] & G[0]) | (P[3] & P[2] & P[1] & P[0] & C[0]);  
    assign S = P ^ C;  
  
    assign PG = P[3] & P[2] & P[1] & P[0];  
    assign GG = G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3]  
& P[2] & P[1] & G[0]);  
endmodule
```

Test Bench : 4 Bit CLA

```
module Test_CLA_4bit;  
    // Inputs  
    reg [3:0] A;
```

```

reg [3:0] B;
reg Cin;

// Outputs
wire [3:0] S;
wire Cout;
wire PG;
wire GG;

// Instantiate the Unit Under Test (UUT)
CLA_4bit uut (
.S(S),
.Cout(Cout),
.PG(PG),
.GG(GG),
.A(A),

.B(B),
.Cin(Cin)
);

initial begin
// Initialize Inputs
A = 0; B = 0; Cin = 0;
// Wait 100 ns for global reset to finish
#100;

// Add stimulus here
A=4'b0001;B=4'b0000;Cin=1'b0;
#10 A=4'b100;B=4'b0011;Cin=1'b0;
#10 A=4'b1101;B=4'b1010;Cin=1'b1;
#10 A=4'b1110;B=4'b1001;Cin=1'b0;
#10 A=4'b1111;B=4'b1010;Cin=1'b0;
end

initial begin
$monitor("time=", $time,, "A=%b B=%b Cin=%b : Sum=%b Cout=%b PG=%b GG=%b", A, B, Cin, S, Cout, PG, GG);
end
endmodule

```

Simulation Results

```
time = 0 A=0000 B=0000 Cin=0 : Sum=0000 Cout=0 PG=0 GG=0
time = 100 A=0001 B=0000 Cin=0 : Sum=0001 Cout=0 PG=0 GG=0
time = 110 A=0100 B=0011 Cin=0 : Sum=0111 Cout=0 PG=0 GG=0
time = 120 A=1101 B=1010 Cin=1 : Sum=1000 Cout=1 PG=0 GG=1
time = 130 A=1110 B=1001 Cin=0 : Sum=0111 Cout=1 PG=0 GG=1
time = 140 A=1111 B=1010 Cin=0 : Sum=1001 Cout=1 PG=0 GG=1
```

Verilog code for Carry Save Adder:

```
module carrysave(p0,p1,p2,p3,p4,p5,s,c,a,b);
output [5:0]p0,p1,p2,p3,p4,p5;
output [10:0]s;
output [7:0]c;
input [5:0]a,b;
wire
d,d1,d2,d3,d4,d5,d6,d7,d8,d9,d10,d11,d12,d13,d14,d15,d16,d17,e1,e2,e3,e4,e5,e6,e7,e8,e
9,e10,e11,e13,e14,e15,e16,e17;

assign p0=b[0]?a:0;
assign p1=b[1]?a:0;
assign p2=b[2]?a:0;
assign p3=b[3]?a:0;
assign p4=b[4]?a:0;
assign p5=b[5]?a:0;
assign s[0]=p0[0];

HA h1(s[1],d,p0[1],p1[0]);
HA h2(e5,d5,p1[5],p2[4]);
FA m1(e1,d1,p0[2],p1[1],p2[0]);
FA m2(e2,d2,p0[3],p1[2],p2[1]);
FA m3(e3,d3,p0[4],p1[3],p2[2]);
FA m4(e4,d4,p0[5],p1[4],p2[3]);

HA h3(e6,d6,p3[1],p4[0]);
HA h4(e11,d11,p4[5],p5[4]);
```

```
FA m5(e7,d7,p3[2],p4[1],p5[0]);
FA m6(e8,d8,p3[3],p4[2],p5[1]);
FA m7(e9,d9,p3[4],p4[3],p5[2]);
FA m8(e10,d10,p3[5],p4[4],p5[3]);
```

```
HA h5(s[2],d12,d,e1);
FA m9(e13,d13,d1,e2,p3[0]);
FA m10(e14,d14,d2,e3,e6);
FA m11(e15,d15,d3,e4,e7);
FA m12(e16,d16,d4,e5,e8);
FA m13(e17,d17,d5,e6,p2[5]);
```

```
HA h6(s[3],c[0],d12,e13);
HA h7(s[4],c[1],d13,e14);
HA h8(s[9],c[6],d10,e11);
HA h9(s[10],c[7],d11,p5[5]);
FA m14(s[5],c[2],d6,d14,e15);
FA m15(s[6],c[3],d7,d15,e16);
FA m16(s[7],c[4],d8,d16,e17);
FA m17(s[8],c[5],d9,d17,e10);
endmodule
```

Address Decoders

- a) 2 to 4 decoder
- b) 3 to 8 decoder
- c) priority encoder

2 : 4 DECODER

VERILOG CODE:

```
module Decoder(A, B, D);

    input A, B;
    output [3:0] D;
    reg [3:0] D;

    always @ (A or B)
    begin
```

```

        if( A == 0 && B == 0 )
            D <= 4'b0001;

        else if ( A == 0 && B == 1 )
            D <= 4'b0010;

        else if ( A == 1 && B == 0 )
            D <= 4'b0100;

        else
            D <= 4'b1000;
    end

endmodule

```

TEST BENCH:

```

module Testbench;

    reg A_t, B_t;
    wire [3:0] D_t;

    Decoder Decoder_1(A_t, B_t, D_t);

    initial
    begin

        //case 0
        A_t <= 0; B_t <= 0;
        #1 $display("D_t = %b", D_t);

        //case 1
        A_t <= 0; B_t <= 1;
        #1 $display("D_t = %b", D_t);

        //case 2
        A_t <= 1; B_t <= 0;
        #1 $display("D_t = %b", D_t);

        //case 3
        A_t <= 1; B_t <= 1;
        #1 $display("D_t = %b", D_t);

    end

endmodule


```

3 : 8 DECODER


Function Table

	Input			Output							
enable	A1	A1	A0	Z7	Z6	Z5	Z4	Z3	Z2	Z1	Z0
0	x	X	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Block Diagram 3-8 line Decoder

 

Circuit Diagram 3-8 line Decoder

 

Verilog Code for 3 to 8 line decoder

```
Module dec(bin,decout,en);
```

```
    input [0:2] bin;
```

```
    input en;
```

```
    output [7:0] decout;
```

```
    reg decout;
```

```
    always @(en or bin)
```

```
    begin
```

```
        decout=0;
```

```
        if(en)
```

```
begin
case(bin)
3'b000:decout=8'o001;
3'b001:decout=8'o002;
3'b010:decout=8'o004;
3'b011:decout=8'o010;
3'b100:decout=8'o020;
3'b101:decout=8'o040;
3'b110:decout=8'o100;
3'b111:decout=8'o200;
endcase
end
end
endmodule
```

(OR)

VERILOG CODE

```
module decodermod(e, a, b, d);

input e;

input a;

input b;

output [7:0] d;
```

```
assign d[0]=(~e)&(~a)&(~b);
```

```
assign d[1]=(~e)&(~a)&(b);
```

```
assign d[2]=(~e)&(a)&(~b);
```

```
assign d[3]=(~e)&(a)&(b);
```

```
assign d[4]=(e)&(~a)&(~b);
```

```
assign d[5]=(e)&(~a)&(b);
```

```
assign d[6]=(e)&(a)&(~b);
```

```
assign d[7]=(e)&(a)&(b);
```

```
endmodule
```

TEST BENCH

```
module decodert_b;
```

```
reg e;
```

```
reg a;
```

```
reg b;
```

```
wire [7:0] d;
```

```
decodermod uut ( .e(e),.a(a),.b(b),.d(d) );
```

```
initial begin
```

```
#10 e=1'b0;a=1'b0;b=1'b0;
```

```

#10 e=1'b0;a=1'b0;b=1'b1;

#10 e=1'b0;a=1'b1;b=1'b0;

#10 e=1'b0;a=1'b1;b=1'b1;

#10 e=1'b1;a=1'b0;b=1'b0;

#10 e=1'b1;a=1'b0;b=1'b1;

#10 e=1'b1;a=1'b1;b=1'b0;

#10 e=1'b1;a=1'b1;b=1'b1;

#10$stop;


end

endmodule

```

4 Bit Priority Encoder in Verilog

Priority Encoder is an encoder circuit that includes a priority function. The operation is such that if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence. Here, the priority decreases from right to left in the input. D[3] has the highest priority. V indicate the validity of the input (atleast one input should be 1) and the Y gives the output.(01 means 1, 10 means 2 like that...)

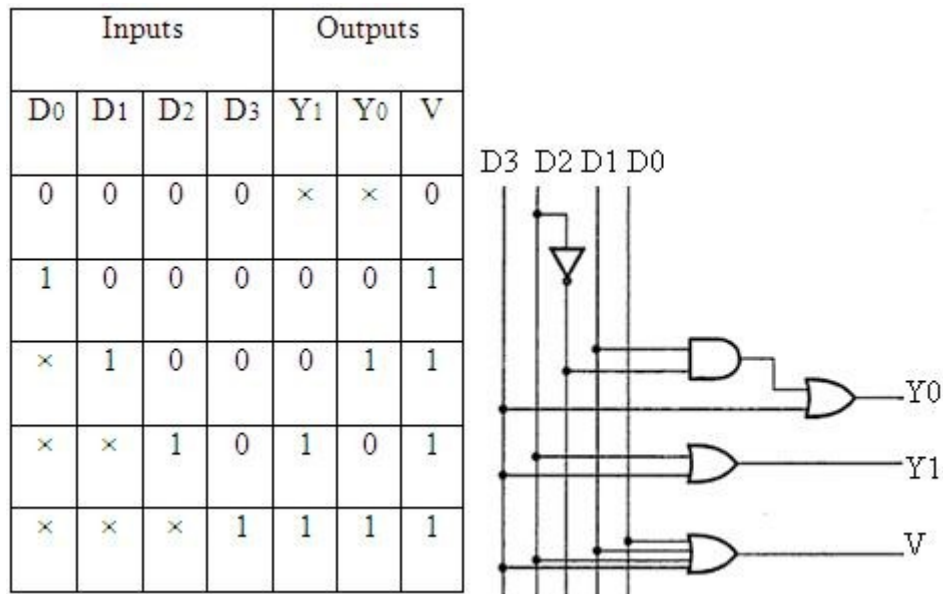

Behavioural Model : 4 Bit Priority Encoder

```

module PriorityEncoder_4Bit(
    input [0:3] D,
    output [1:0] Y,
    output V
);
    reg [1:0] Y;
    reg V;
    always @(D)
    begin
        Y[1] <= D[2] | D[3];
        Y[0] <= D[3] | D[1] & ~D[2];
        V = D[0] | D[1] | D[2] | D[3];
    end
endmodule

```

Test Bench : 4 Bit Priority Encoder

```

module PriorityEncoder_4Bit_Test;
    // Inputs
    reg [3:0] D;
    // Outputs

```

```

wire [1:0] Y;
wire V;
// Instantiate the Unit Under Test (UUT)
PriorityEncoder_4Bit uut (
    .D(D),
    .Y(Y),
    .V(V)
);
initial begin
    // Initialize Inputs
    D = 0;
    // Wait 100 ns for global reset to finish
    #100;
    // Add stimulus here
    #10 D = 4'b0000;
    #10 D = 4'b1000;
    #10 D = 4'b0100;
    #10 D = 4'b0010;
    #10 D = 4'b0001;
    #10 D = 4'b1010;
    #10 D = 4'b1111;
end
initial begin
    $monitor("time=", $time, , "D=%b : Y=%b V=%b", D, Y, V);
end
endmodule

```

Simulation Results

```

time= 000, D=0000 : Y=00 V=0
time= 120, D=1000 : Y=00 V=1
time= 130, D=0100 : Y=01 V=1
time= 140, D=0010 : Y=10 V=1
time= 150, D=0001 : Y=11 V=1
time= 160, D=1010 : Y=10 V=1
time= 170, D=1111 : Y=11 V=1

```


MULTIPLEXERS

4 : 1 MULTIPLEXER


Function Table

Selection Inputs		Output
S1	S0	
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Block Diagram 4:1 Multiplexer

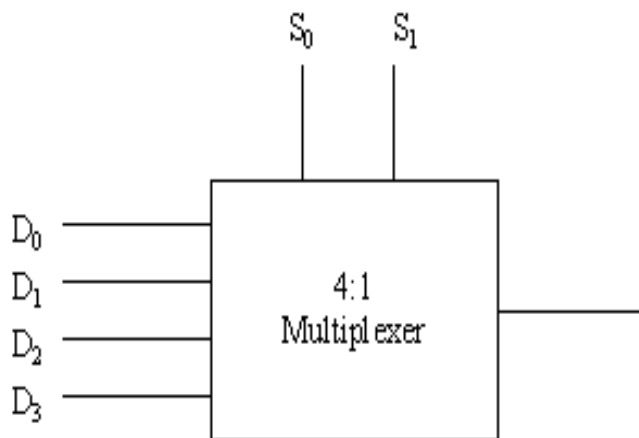

Circuit Diagram 4:1 Multiplexer

 

Verilog code 4 to 1 for multiplexer

```
module mux4to1(Y, I0,I1,I2,I3, sel);
```

```
    output Y;
```

```
    input I0,I1,I2,I3;
```

```
    input [1:0] sel;
```

```
    reg Y;
```

```
    always @ (sel or I0 or I1 or I2 or I3)
```

```
    case (sel)
```

```
        2'b00:Y=I0;
```

```
        2'b01:Y=I1;
```

```
        2'b10: Y=I2;
```

```
        2'b11: Y=I3;
```



```
        default: Y=2b'00;
endcase
endmodule
```

(OR)

VERILOG CODE:

```
module mux4bit(a, s, o);

input [3:0] a;

input [1:0] s;

output o;

reg o;

always @(a or s)

begin

case (s)

2'b00:o=a[0];

2'b01:o=a[1];

2'b10:o=a[2];

2'b11:o=a[3];

default:o=0;

endcase
```

end

endmodule

TEST BENCH:

module muxt_b;

reg [3:0] a;

reg [1:0] s;

wire o;

mux4bit uut (.a(a), .s(s),.o(o));

initial begin

#10 a=4'b1010;

#10 s=2'b00;

#10 s=2'b01;

#10 s=2'b10;

#10 s=2'b11;

#10 \$stop;

end

endmodule

1:4 Demultiplexer


Function table

Data Input	Selection Input		Output			
D	S1	S0	Y3	Y2	Y1	Y0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


Function Table

Inputs		Output
S ₁	S ₀	
0	0	Y ₀ =D
0	1	Y ₁ =D
1	0	Y ₂ =D
1	1	Y ₃ =D

Block Diagram 1:4 Demultiplexer

 

Circuit Diagram 1:4 Demultiplexer

 

Verilog code for 1 to 4 demultiplexer

```
module demux(S,D,Y);
```

```
    Input [1:0] S;
```

```
    Input D;
```

```
    Output [3:0] Y;
```

```
    reg Y;
```

```
    always @(S OR D)
```

```
    case({D,S})
```

```
        3'b100:Y=4'b0001;
```

```
        3'b101:Y=4'b0010;
```

```

        3'b110:Y=4'b0100;

        3'b111:Y=4'b1000;

        default:Y=4'b0000;

    endcase
endmodule

```

TEST BENCH:

```

#10 s=2'b00;

#10 s=2'b01;

#10 s=2'b10;

#10 s=2'b11;

#10 $stop;

end

endmodule

```

COUNTERS


4-Bit Binary Ripple Counter

Function Table

Output(count 0-15)

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Circuit Diagram

 

Verilog Code for Ripple Counter

```

module ripple(clkr,st,,t,A,B,C,D);
input clk,rst,t;
output A,B,C,D;

```

```

Tff T0(D,clk,rst,t);
Tff T1(C,clk,rst,t);
Tff T2(B,clk,rst,t);
Tff T3(A,clk,rst,t);
endmodule

module Tff(q,clk,rst,t);
input clk,rst,t;
output q;
reg q;
always @(posedge clk)
begin
if(rst)
q<=1'b0;
else
if(t)
q<=~q;
end
endmodule

```


4-bit Up-Down Counter

Count Table

Output(count	Output (count up)
--------------	-------------------

down)							
Q0	Q1	Q2	Q3	Q0	Q1	Q2	Q3
1	1	1	1	0	0	0	0
1	1	1	0	0	0	0	1
1	1	0	1	0	0	1	0
1	1	0	0	0	0	1	1
1	0	1	1	0	1	0	0
1	0	1	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	0	0	0	1	1	1
0	1	1	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	0	1	1	0	1	0
0	1	0	0	1	0	1	1
0	0	1	1	1	1	0	0
0	0	1	0	1	1	0	1
0	0	0	1	1	1	1	0
0	0	0	0	1	1	1	1

A four-bit synchronous "up/down" counter

 

```

module updowncount (R, Clock, clr, E, up_down, Q);
parameter n = 4;
input [n-1:0] R;
input Clock, clr, E, up_down;
output [n-1:0] Q;
reg [n-1:0] Q;
integer direction;

always @(posedge Clock)
begin
if (up_down) direction = 1;
else direction = -1;

if (clr) Q <= R;
else if (E) Q <= Q + direction;
end
endmodule

```

end

endmodule

(OR)

UP-DOWNCOUNTER VERIOLG CODE

```
module updowncounterm0d(clk, clear, updown, q);
```

```
input clk;
```

```
input clear;
```

```
input updown;
```

```
output [3:0] q;
```

```
reg [3:0] q;
```

```
always@(posedge clear or posedge clk)
```

```
begin
```

```
if(clear)
```

```
q <= 4'b0000;
```

```
else if(updown)
```

```
q <= q+1'b1;
```

```
else
```

```
q <= q-1'b1;
```

```
end
```

```
endmodule
```

TEST BENCH

```
module updowncountert_b;
```

```
reg clk;
```

```
reg clear;
```

```
reg updown;
```

```
wire [3:0] q;
```

```
updowncountertmod uut (.clk(clk),.clear(clear), .updown(updown), .q(q) );
```

```
initial begin
```

```
clk = 0;
```

```
clear = 0;
```

```
updown = 0;
```

```
#5 clear=1'b1;
```

```
#5 clear=1'b0;
```

```
#100 updown=1'b1;
```

end



always #5 clk=~clk;

initial #150 \$stop;

endmodule

Ring Counter

Circuit Diagram for ring counter

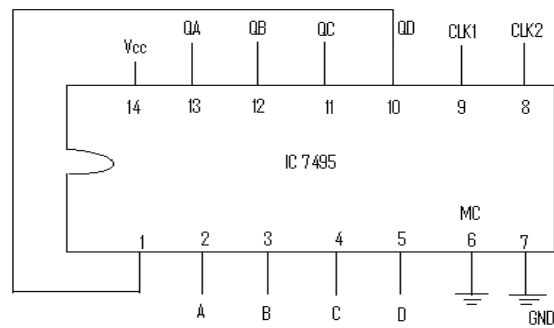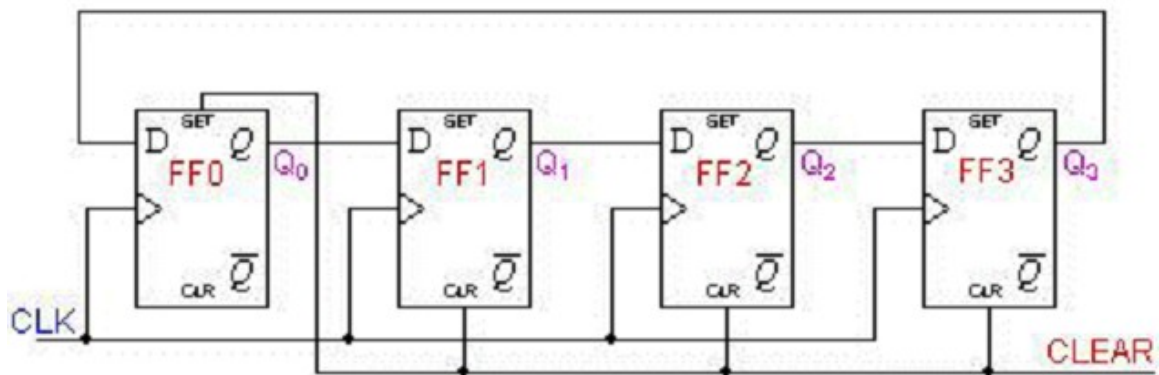

Count Table

Verilog code for ring counter

	clk	Q _a	Q _b	Q _c	Q _d
	1	1	0	0	0
input	2	0	1	0	0
output	3	0	0	1	0
reg [n-	4	0	0	0	1

module ring_count (Resetn, Clock, Q);
 parameter n = 5;
 Resetn, Clock;
 [n-1:0] Q;
 1:0] Q;
 always @(posedge Clock)
 if (!Resetn)
 begin
 Q[4:1] <= 0;

```

Q[0] <= 1;

end

else



Q <= {{Q[3:0]}, {Q[4]}};

endmodule

```


Johnson Counter

Circuit Diagram for Johnson counter

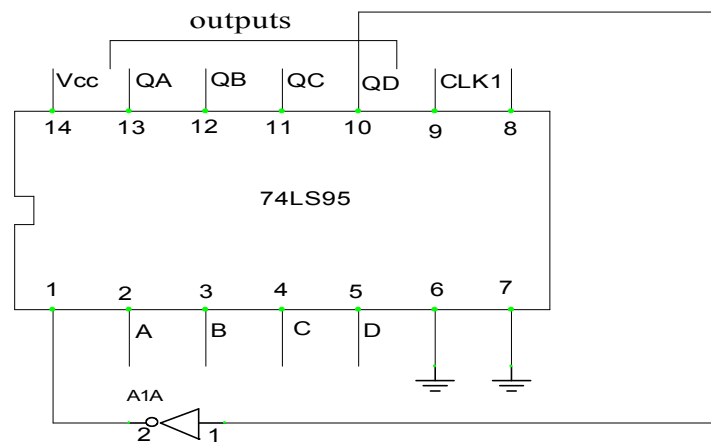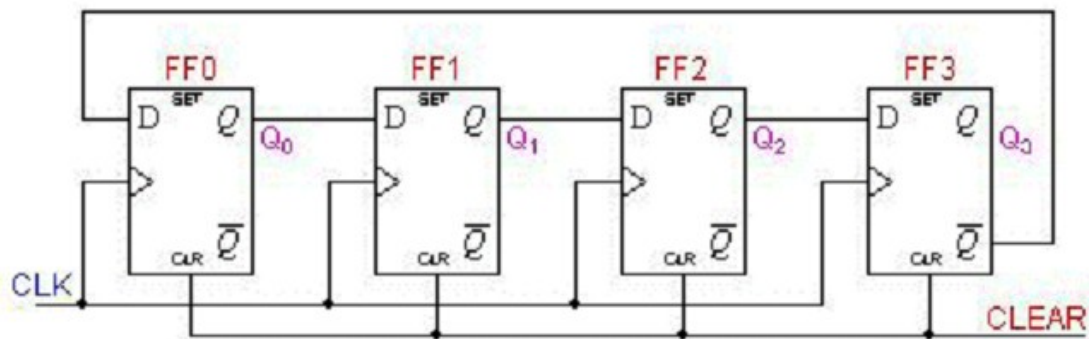

Count Table

Clock Pulse	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	1	1	1
4	1	1	1	1
5	1	1	1	0
6	1	1	0	0
7	1	0	0	0



Verilog code

```
module stc(clk,clr,q,r,s,t);
```

```
input clk,clr;  
output q,r,s,t;
```

```
reg q,r,s,t;
```

```
always@(negedge clk)
```

```
begin
```

```
if(~clr)
```

```
begin
```

```
q=1'b0;
```

```
end
```

```
else
```

```
begin
```

```
q<=~t;
```

```
r<=q;
```

```
s<=r;
```

```
t<=s;
```


```
end
```

```
end
```

endmodule

Pseudo Random Sequence Generator in Verilog

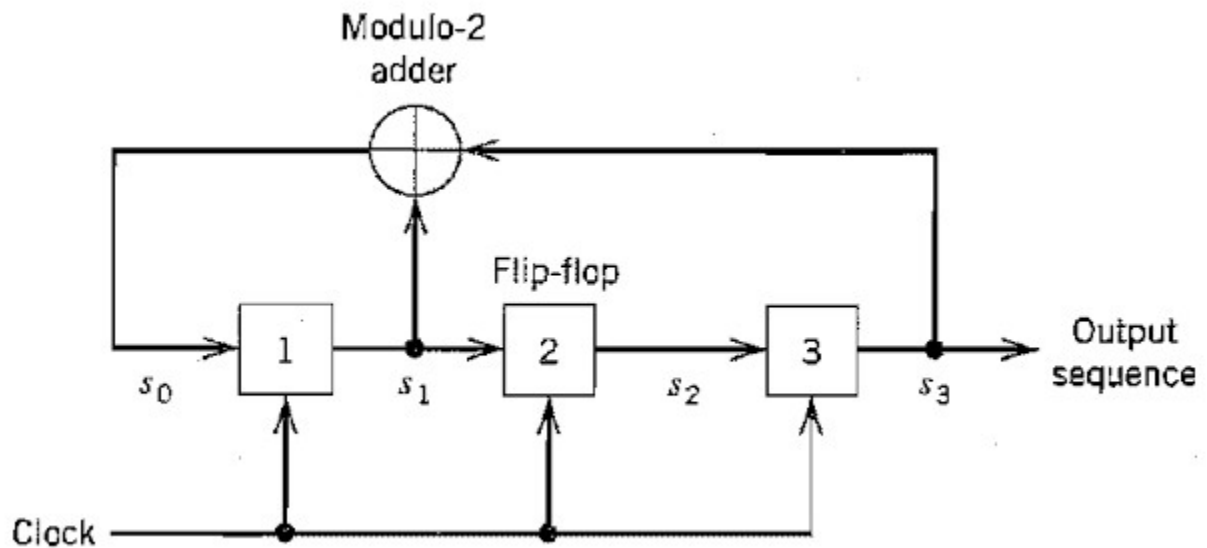Pseudo Random Sequence is widely used in spread spectrum communication, to spread and de-spread the information sequence. The following diagram shows a PN sequence generator which has 3 memory elements, leads to processing gain 7 ($2^3 - 1$). According to the diagram, if the initial state is all zero, then the sequence will also be all zeros which is not usable.



Behavioural Model

```
module PNSeqGen(  
    input clk, reset,  
    output s3  
);  
    reg s1, s2, s3;
```



```

wire s0;
// MODULO 2 ADDITION
assign s0 = s1 ^ s3;
// STATE MACHINE
always @ (posedge clk or reset) begin
    // INITIAL STATE SHOULDN'T BE 000 => 100
    if(reset) begin
        s1 <= 1;
        s2 <= 0;
        s3 <= 0;
    end else begin
        s1 <= s0;
        s2 <= s1;
        s3 <= s2;
    end
end
endmodule

```

Test Bench

```

module Test_PNSeqGen;
    // Inputs
    reg clk;
    reg reset;
    // Outputs
    wire s3;
    // Instantiate the Unit Under Test (UUT)
    PNSeqGen uut (
        .clk(clk),
        .reset(reset),
        .s3(s3)
    );
    initial begin
        // Initialize Inputs
        clk = 0;
        reset = 0;
        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
        #10 reset = 1;
        #10 reset = 0;
        #200 $finish;
    end
    always begin
        #5 clk = ~clk;
    end
end

```

```
// PRINT SEQUENCE
always @ (posedge clk) $write("%b",s3);
endmodule
```

Output

```
001110100111010011101
```

ACCUMULATOR VERILOG CODE

```
module accumod (in, acc, clk, reset);
```

```
input [7:0] in;
```

```
input clk, reset;
```

```
output [7:0] acc;
```

```
reg [7:0] acc;
```

```
always@(clk) begin
```

```
if(reset)
```

```
acc <= 8'b00000000;
```

```
else
```

```
acc <= acc + in;
```

```
end
```

```
endmodule
```

TEST BENCH

```
module accunt_b;

reg [7:0] in;

reg clk;

reg reset;

wire [7:0] acc;

accumod uut ( .in(in), .acc(acc),.clk(clk),.reset(reset) );

initial begin

#5 reset<=1'b1;

#5 reset<=1'b0;

clk =1'b0;

in = 8'b00000001;

#50 in = 8'b00000010;

#50 in = 8'b00000011;

end

always #10 clk = ~clk;

initial#180 $stop;
```

endmodule

Implementation of 4-bit Magnitude Comparator

Consider two 4-bit binary numbers A and B such that

$$A = A_3A_2A_1A_0$$

$$B = B_3B_2B_1B_0$$


$$x_i = A_i \cdot B_i + \overline{A_i} \cdot \overline{B_i}$$

$$(A = B) = x_3x_2x_1x_0$$

$$(A > B) = A_3 \cdot \overline{B_3} + x_3A_2\overline{B_2} + x_3x_2A_1\overline{B_1} + x_3x_2x_1A_0\overline{B_0}$$

$$(A < B) = \overline{A_3} \cdot B_3 + x_3\overline{A_2}B_2 + x_3x_2\overline{A_1}B_1 + x_3x_2x_1\overline{A_0}B_0$$

Circuit Diagram

 

4-Bit Magnitude Comparator

Verilog code(Abstract level)

```
module compare(A,B,y);
```

```
input [3:0] A,B;
```

```
output [2:0] y;
```

```
reg y;
```

```
always @(A or B)
```

```
if(A==B)
```

```
y=3'b001;
```

```
else if(A<B)
```

```
y=3'b010;
```

else

y=3'b100;

endmodule

Verilog code for 4-bit magnitude comparator

```
module compare(A,B,x,y,z);
```

```
input [3:0] A,B;
```

```
output x, y,z;
```

```
wire x0,x1,x2,x3;
```

```
assign x0=((~A[0]&B[0])| (A[0]&~B[0]));
```

```
assign x1=((~A[1]&B[1])| (A[1]&~B[1]));
```

```
assign x2=((~A[2]&B[2])| (A[2]&~B[2]));
```

```
assign x3=((~A[3]&B[3])| (A[3]&~B[3]));
```

```
assign x=x0&x1&x2&x3;
```

```
assign y=((A[3]&~B[3])|(x3&A[2]&~B[2])|(x3&x2&A[1]&~B[1])|(x3&x2&x1&A[0]&~B[0]));
```

```
assign z=((~A[3]&B[3])|(x3&~A[2]&B[2])|(x3&x2&~A[1]&B[1])|(x3&x2&x1&~A[0]&B[0]));
```

```
endmodule
```

DESIGN OF MODIFIED BOOTH MULTIPLIER

AIM:

To design a modified booth multiplier in Verilog and to simulate & synthesis the same using XILINX ISE Tool.

THEORY:

Bit Pair Encoding (BPE) is a modified booth multiplication technique where the number of additions (no of partial products so generated) is reduced from n to n/2 for an 'n' bit multiplier.

Bit pair encoding of a multiplier examines 3 bits at a time and creates a 2-bit code whose values determines whether to

Add the multiplicand
 Shift the multiplicand by 1 bit and then add
 Subtract the multiplicand (adding 2s complement of the multiplicand to the product)
 Shift the 2s complement of the multiplicand to the left by 1 bit and then add
 To only shift the multiplicand to the location corresponding to the next bit-pair.

The first step of BPE algorithm is seeded with a value of 0 in the register cell to the right of the LSB of the multiplier word. Subsequent actions depend on the value of the recoded bit-pair. The index 'i' increments by two until the word is exhausted. If the word contains an odd number of bits, its sign bit must be extended by one bit to accommodate the recoding scheme. Recoding divides the multiplier word by 2, so the number of possible additions is reduced by a factor of 2. The rules for bit-pair encoding are summarized in the table provided in the left.

SOURCE CODE:

```
module booth #(parameter WIDTH=4)
( input  clk,
  input  enable,
  input  [WIDTH-1:0] multiplier,
  input  [WIDTH-1:0] multiplicand,
  output reg [2*WIDTH-1:0] product);

parameter IDLE = 2'b00,          // state encodings
          ADD  = 2'b01,
          SHIFT = 2'b10,
          OUTPUT = 2'b11;

reg [1:0]  current_state, next_state; // state registers.
reg [2*WIDTH+1:0] a_reg,s_reg,p_reg,sum_reg; // computational values.
reg [WIDTH-1:0]  iter_cnt; // iteration count for determining when done.
wire [WIDTH:0]   multiplier_neg; // negative value of multiplier

always @(posedge clk)
  if (!enable) current_state = IDLE;
  else        current_state = next_state;

always @* begin
  next_state = 2'bx;
  case (current_state)
    IDLE: if (enable) next_state = ADD;
          else next_state = IDLE;
    ADD:  next_state = SHIFT;
    SHIFT: if (iter_cnt==WIDTH) next_state = OUTPUT;
           else next_state = ADD;
    OUTPUT: next_state = IDLE;
  endcase
end
```

```

endcase
end

// negative value of multiplier.
assign multiplier_neg = -{multiplier[WIDTH-1],multiplier};

// algorithm implemenation details.
always @(posedge clk) begin
  case (current_state)
    IDLE : begin
      a_reg  <= {multiplier[WIDTH-1],multiplier,{(WIDTH+1){1'b0}}};
      s_reg  <= {multiplier_neg,{(WIDTH+1){1'b0}}};
      p_reg  <= {{(WIDTH+1){1'b0}},multiplicand,1'b0};
      iter_cnt <= 0;
    end
    ADD : begin
      case (p_reg[1:0])
        2'b01 : sum_reg <= p_reg+a_reg;
        2'b10 : sum_reg <= p_reg+s_reg;
        2'b00,2'b11 : sum_reg <= p_reg;
      endcase
      iter_cnt <= iter_cnt + 1;
    end
    SHIFT : begin
      p_reg <= {sum_reg[2*WIDTH+1],sum_reg[2*WIDTH+1:1]};
    end
    OUTPUT: product = p_reg>>1;
  endcase
end//always ends

endmodule //end of source code

```

TEST BENCH:

```

module testbench;
  // Inputs
  reg clk;
  reg enable;
  reg [3:0] multiplier;
  reg [3:0] multiplicand;
  // Outputs
  wire done;
  wire [7:0] product;

```



```

// Instantiate the Unit Under Test (UUT)
booth uut (
    .clk(clk),
    .enable(enable),
    .multiplier(multiplier),
    .multiplicand(multiplicand),
    .product(product)
);

initial
    clk=1'b0;
always
    #5    clk=~clk;

initial begin
    enable = 0;
    multiplier = 0;
    multiplicand = 0;

#250 enable = 1;
    multiplier = 4'b0011;
    multiplicand = 4'b0011;

#250 enable = 1;
    multiplier = 4'b1010;
    multiplicand = 4'b0100;

#250 enable = 1;
    multiplier = 4'b0010;
    multiplicand = 4'b1001;

#250 enable = 1;
    multiplier = 4'b1010;
    multiplicand = 4'b1100;
#250;
end
endmodule //end of testbench

```



(OR)

BOOTH'S MULTIPLIER

VERILOG CODE:

```
module multiplier(prod, busy, mc, mp, clk, start);
output [15:0] prod;
output busy;
input [7:0] mc, mp;
input clk, start;
reg [7:0] A, Q, M;
reg Q_1;
reg [3:0] count;
wire [7:0] sum, difference;
always @(posedge clk)
begin
    if (start) begin
        A <= 8'b0;
        M <= mc;
        Q <= mp;
        Q_1 <= 1'b0;
        count <= 4'b0;
    end
    else begin
        case ({Q[0], Q_1})
            2'b0_1 : {A, Q, Q_1} <= {sum[7], sum, Q};
            2'b1_0 : {A, Q, Q_1} <= {difference[7], difference, Q};
```

```

        default: {A, Q, Q_1} <= {A[7], A, Q};
    endcase

    count <= count + 1'b1;

end

end

alu adder (sum, A, M, 1'b0); );//MODULE INSTANTIATION
//alu subtracter (difference, A, ~M, 1'b1); );//MODULE INSTANTIATION
assign prod = {A, Q};
assign busy = (count < 8);
endmodule

```

//The following is an alu.

//It is an adder, but capable of subtraction:

//Recall that subtraction means adding the two's complement--

// $a - b = a + (-b) = a + (\text{inverted } b + 1)$

//The 1 will be coming in as cin (carry-in)

```

module alu(out, a, b, cin);
    output [7:0] out;
    input [7:0] a;
    input [7:0] b;
    input cin;
    assign out = a + b + cin;
endmodule

```

TEST BENCH:

```
module testbench;
reg clk, start;
reg [7:0] a, b;
wire [15:0] ab;
wire busy;
multiplier multiplier1(ab, busy, a, b, clk, start);//MODULE INSTANTIATION
initial begin
clk = 0;
$display("first example: a = 3 b = 17");
a = 3; b = 17; start = 1; #50 start = 0;
#80 $display("first example done");
$display("second example: a = 7 b = 7");
a = 7; b = 7; start = 1; #50 start = 0;
#80 $display("second example done");
$finish;
end
always #5 clk = !clk;
always @(posedge clk) $strobe("ab: %d busy: %d at time=%t", ab, busy, $stime);
endmodule
```

OUTPUT:

```
first example: a = 3 b = 17
ab: 17 busy: 1 at time=
```

ab: 17 busy: 1 at time=	15
ab: 17 busy: 1 at time=	25
ab: 17 busy: 1 at time=	35
ab: 17 busy: 1 at time=	45
ab: 65160 busy: 1 at time=	55
ab: 196 busy: 1 at time=	65
ab: 98 busy: 1 at time=	75
ab: 49 busy: 1 at time=	85
ab: 65176 busy: 1 at time=	95
ab: 204 busy: 1 at time=	105
ab: 102 busy: 1 at time=	115
ab: 51 busy: 0 at time=	125

first example done


second example: $a = 7$ $b = 7$

ab: 7 busy: 1 at time=	135
ab: 7 busy: 1 at time=	145
ab: 7 busy: 1 at time=	155
ab: 7 busy: 1 at time=	165
ab: 7 busy: 1 at time=	175
ab: 64643 busy: 1 at time=	185
ab: 65089 busy: 1 at time=	195
ab: 65312 busy: 1 at time=	205
ab: 784 busy: 1 at time=	215
ab: 392 busy: 1 at time=	225
ab: 196 busy: 1 at time=	235
ab: 98 busy: 1 at time=	245
ab: 49 busy: 0 at time=	255

second example done

wave - default

File Edit Cursor Zoom Format Window

 

● /testbench/clock	1	
● /testbench/start	0	
⊕ /testbench/a	000000011	000000011
⊕ /testbench/b	00010001	00010001
⊕ /testbench/ab	1111111010011000	10000000001100010
● /testbench/busy	Srl	
⊕ /testbench/multiplier /prod	1111111010011000	10000000001100010
● /testbench/multiplier1 /busy	Srl	
⊕ /testbench/multiplier1 /mc	000000011	000000011
⊕ /testbench/multiplier1 /mp	00010001	00010001
● /testbench/multiplier1 /clk	Srl	
● /testbench/multiplier1 /start	Srl	
⊕ /testbench/multiplier1 /A	111111110	
⊕ /testbench/multiplier1 /Q	10011000	
⊕ /testbench/multiplier1 /M	000000011	
● /testbench/multiplier1 /Q_1	1	
⊕ /testbench/multiplier1 /count	0101	
⊕ /testbench/multiplier1 /sum	00000001	
⊕ /testbench/multiplier1 /difference	111111011	
⊕ /testbench/multiplier1 /adder/out	00000001	
⊕ /testbench/multiplier1 /adder/a	111111110	
⊕ /testbench/multiplier1 /adder/b	000000011	
● /testbench/multiplier1 /adder/cin	Srl	
⊕ /testbench/multiplier1 /subtractor/out	111111011	
⊕ /testbench/multiplier1 /subtractor/a	111111110	
⊕ /testbench/multiplier1 /subtractor/b	1111111100	

